


Key Points

- terminology – logic gates, logic circuits, combinatorial logic circuit, feedback loop, disjunctive normal form
- processes / algorithms
 - building a logic circuit from a proposition
 - constructing a proposition from a logic circuit
 - using boolean algebra to simplify circuits
- theorems
 - every compound proposition is computed by a logic circuit with one output wire
 - every combinatorial logic circuit with one output computes the value of some compound proposition
 - it is possible to build a proposition with only \wedge , \vee , \neg and in disjunctive normal form for any truth table where at least one of the output values is true
- applications to computers

33


Logic Circuits

 - logic gates* are electronic components that compute values of simple propositions



- input and output wires can be in one of two states (on, off), which corresponds to the boolean values \mathbb{T} , \mathbb{F}

- logic circuits* are built from connecting inputs and outputs of logic gates to each other

 

CPSC 229: Foundations of Computation • Spring 2024

34

Constructing Circuits From Propositions

- algorithm
 - if the proposition contains operators other than \wedge , \vee , \neg , convert the proposition to a logically equivalent one using only \wedge , \vee , \neg
 - determine the *main operator* – the one that is applied last
 - add the corresponding logic gate to the circuit
 - repeat the last two steps for each of the compound propositions joined by this main operator, connecting their outputs to the inputs of this main operator
 - create one input for each propositional variable and connect them to the appropriate inputs


| | |
|--|---|
| a) $A \wedge (B \vee \neg C)$ | b) $(p \wedge q) \wedge \neg(p \wedge \neg q)$ |
| c) $(p \vee q \vee r) \wedge (\neg p \vee \neg q \vee \neg r)$ | d) $\neg(A \wedge (B \vee C)) \vee (B \wedge \neg A)$ |

CPSC 229: Foundations of Computation • Spring 2024

35

Constructing Circuits From Propositions

| | |
|--|---|
| a) $A \wedge (B \vee \neg C)$ | b) $(p \wedge q) \wedge \neg(p \wedge \neg q)$ |
| c) $(p \vee q \vee r) \wedge (\neg p \vee \neg q \vee \neg r)$ | d) $\neg(A \wedge (B \vee C)) \vee (B \wedge \neg A)$ |

 


CPSC 229: Foundations of Computation • Spring 2024

36


Constructing Propositions From Circuits

 - algorithm
 - label the circuit's inputs with the name of a propositional variable
 - label each gate's output with the proposition consisting of the propositions represented by the gate's inputs combined with operator represented by the gate
 - the output from the final logic gate is the proposition




Simplifying Circuits

 - algorithm
 - convert the circuit to propositional logic
 - use boolean algebra to simplify the proposition
 - construct the circuit corresponding to the simplified proposition



Simplifying Circuits

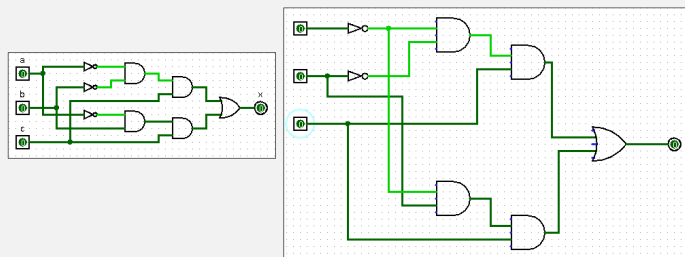- also be alert to the possibility of reusing outputs from gates



Theorems

- every compound proposition is computed by a logic circuit with one output wire
- rationale
 - apply the algorithm for converting propositions into circuits

Theorems

- [theorem 1.3] it is possible to build a proposition with only \wedge, \vee, \neg and in disjunctive normal form for any truth table where at least one of the output values is true
 - what if all of the output values are false?

| p | q | r | output |
|---|---|---|--------|
| F | F | F | F |
| F | F | T | F |
| F | T | F | F |
| F | T | T | F |
| T | F | F | F |
| T | F | T | F |
| T | T | F | F |
| T | T | T | F |

this is a contradiction – not really useful to express

workaround: accept \perp as a proposition in disjunctive normal form

Applications to Computers

Why use logic circuits in computers?

- on, off can be interpreted as 1, 0
- numbers can be represented in binary

| | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 2^7 | 2^6 | 2^5 | 2^4 | 2^3 | 2^2 | 2^1 | 2^0 |
| x128 | x64 | x32 | x16 | x8 | x4 | x2 | x1 |
| 64 | + | | | | 4 | + | 2 |
| 70 | | | | | | | |


- arithmetic can be performed on numbers
 - can create truth tables which correspond to arithmetic involving binary numbers
 - theorem 1.3 means a logic circuit can be constructed for those truth tables
 - actually carrying out that process may only be practical for small circuits, but the goal of the proof is that it is possible

Half Adder

- for adding two 1-bit numbers

| | | |
|-----|-----|-----|
| 1) | 2) | 3) |
| 0 | 0 | 1 |
| + 0 | + 1 | + 0 |
| 0 | 1 | 1 |
| | | 10 |

the definition

 

corresponding circuit (half adder)

the corresponding truth table


| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

propositions corresponding to the truth table

sum bit
 $(\neg A \wedge B) \vee (A \wedge \neg B)$
 $\equiv A \oplus B$
 carry bit
 $(A \wedge B)$

Full Adder

 - after the first (rightmost) column, each column involves adding three bits
 - the current bit from each number (A and B), plus the carry bit from the column to the right (Cin)



| Input | | | Output | |
|-------|---|-----|--------|-------|
| A | B | Cin | Sum | Carry |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

truth table for adding three bits

Full Adder

| Input | | | Output | |
|-------|---|-----------------|--------|-------|
| A | B | C _{in} | Sum | Carry |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

propositions corresponding to the truth table

sum bit
 $(\neg A \wedge \neg B \wedge C_{in}) \vee$
 $(\neg A \wedge B \wedge \neg C_{in}) \vee$
 $(A \wedge \neg B \wedge \neg C_{in}) \vee$
 $(A \wedge B \wedge C_{in})$


carry bit
 $(\neg A \wedge B \wedge C_{in}) \vee$
 $(A \wedge \neg B \wedge C_{in}) \vee$
 $(A \wedge B \wedge \neg C_{in}) \vee$
 $(A \wedge B \wedge C_{in})$



can use boolean algebra to simplify these propositions to

sum bit $-(A \oplus B) \oplus C_{in}$
 carry bit $-(C_{in} \wedge (A \oplus B)) \vee (B \wedge A)$

← corresponding circuit

 

Adders

- string n full adders together to add n -bit numbers
- e.g. 2-bit adder $A_1 A_0 + B_1 B_0 = S_1 S_0$

